

# Assignment-2

Name:A.Gowri Priya

Email : gowripriyaappayyagari@gmail.com

## Abstract

Reduce the following Boolean Expression to its simplest form using K-Map by using assembly language:  $E(U,V,Z,W) = (2, 3, 6, 8, 9, 10, 11, 12, 13)$

## 1 Components

| Components            | Value   | Quantity |
|-----------------------|---------|----------|
| Arduino               | UNO     | 1        |
| seven segment display | -       | 1        |
| Jumper wires          | M-M     | 18       |
| Breadboard            |         | 1        |
| Resister              | 150 ohm | 1        |
| Decoder               | 7447    | 1        |

## 2 K-Map

From the given data the minterms are 2,3,6,8,9,10,11,12,13.

| ZY | XW |    |    |    |
|----|----|----|----|----|
|    | 00 | 01 | 11 | 10 |
| 00 | 0  | 0  | 1  | 1  |
| 01 | 0  | 0  | 0  | 1  |
| 11 | 1  | 1  | 0  | 0  |
| 10 | 1  | 1  | 1  | 1  |

The minimized expression is  $E = (UZ' + V'Z + U'ZW')$

| ZY | XW |    |    |    |
|----|----|----|----|----|
|    | 00 | 01 | 11 | 10 |
| 00 | 0  | 0  | 1  | 1  |
| 01 | 0  | 0  | 0  | 1  |
| 11 | 1  | 1  | 0  | 0  |
| 10 | 1  | 1  | 1  | 1  |

## 3 HardwareConnections

- \*Make the connections as shown in the Figure3 and Figure4.
- \*Connect COM pin of seven segment display to Vcc through Resister and Dot pin to ground.

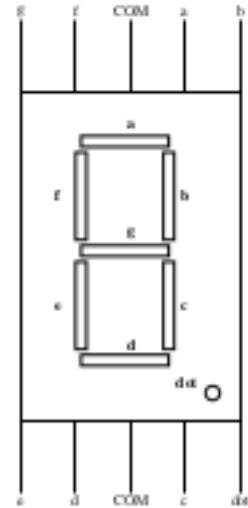


Figure 1: Seven segment display



Figure 2: Pin diagram of 7447IC

| 7447    | $\bar{a}$ | $\bar{b}$ | $\bar{c}$ | $\bar{d}$ | $\bar{e}$ | $\bar{f}$ | $\bar{g}$ |
|---------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Display | a         | b         | c         | d         | e         | f         | g         |

Figure 3:

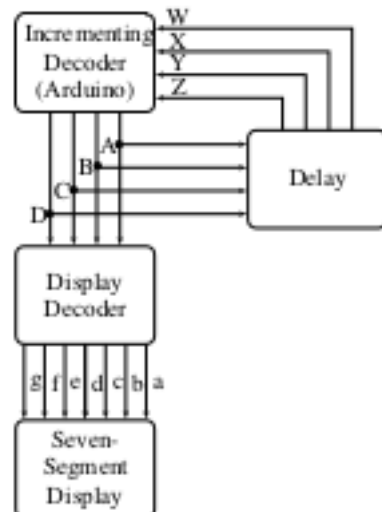


Figure 4:

| U | V | Z | W | E |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

Truth Table

4 Execution

\*Verify the above truth table by using the minimized expression in the following code.

[https://github.com/gowripriya-2002/FWC/blob/main/Asg\\_2/asg\\_2.asm](https://github.com/gowripriya-2002/FWC/blob/main/Asg_2/asg_2.asm)