

Assignment-3

Name:A.Gowri Priya

Email : gowripriyaappayyagari@gmail.com

Abstract

Reduce the following Boolean Expression to its simplest form using K-Map by using assembly language: $E(U,V,Z,W) = (2, 3, 6, 8, 9, 10, 11, 12, 13)$

1 Components

Components	Value	Quantity
Arduino	UNO	1
seven segment display	-	1
Jumper wires	M-M	18
Breadboard		1
Resister	150 ohm	1
Decoder	7447	1

2 K-Map

From the given data the minterms are 2,3,6,8,9,10,11,12,13.

ZY \ XW	00 01 11 10			
	00	01	11	10
00	0	0	1	1
01	0	0	0	1
11	1	1	0	0
10	1	1	1	1

The minimized expression is $E = (UZ' + V'Z + U'ZW')$

ZY \ XW	00 01 11 10			
	00	01	11	10
00	0	0	1	1
01	0	0	0	1
11	1	1	0	0
10	1	1	1	1

3 HardwareConnections

*Make the connections as shown in the Figure3 and Figure4.

*Connect COM pin of seven segment display to Vcc through Resister and Dot pin to ground.

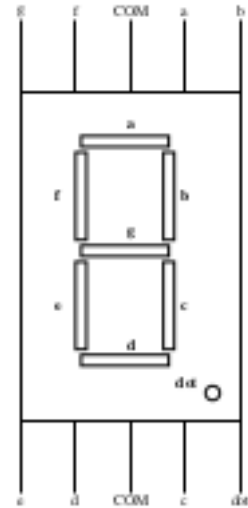


Figure 1: Seven segment display



Figure 2: Pin diagram of 7447IC

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Figure 3:

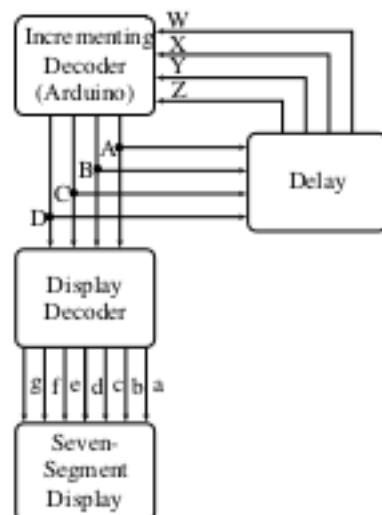


Figure 4:

U	V	Z	W	E
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Truth Table

4 Execution

*Verify the above truth table by using the minimized expression in the following code.

https://github.com/gowripriya-2002/FWC/blob/main/Asg-3/asg_3.c